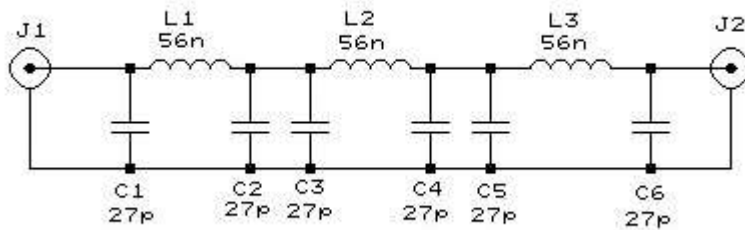


LOWPASS FILTER 150 MHz



P1 SMA male for PCB Amphenol 132365-10 (Digikey ACX1915-ND)

P2 SMA female for PCB Amphenol 132357-11 (Digikey ACX1911-ND)


C1-C6 27pF COG/NPO 250V Size 805 (Farnell 1885439)



L1-L3 56nH Neosid SMD coil 00610235 or homemade (see below)



Wire size 0.4 mm CuL

MEASUREMENTS (made with HP8712B)

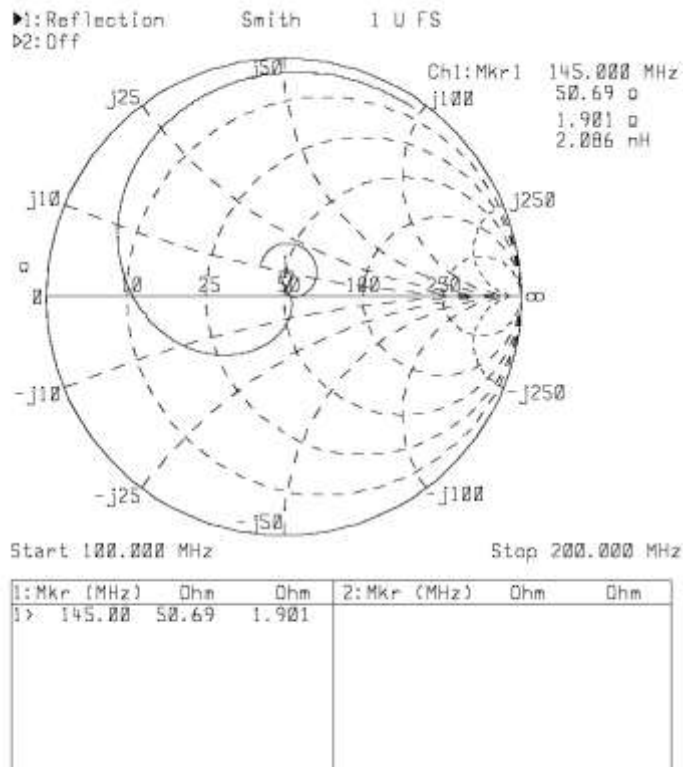

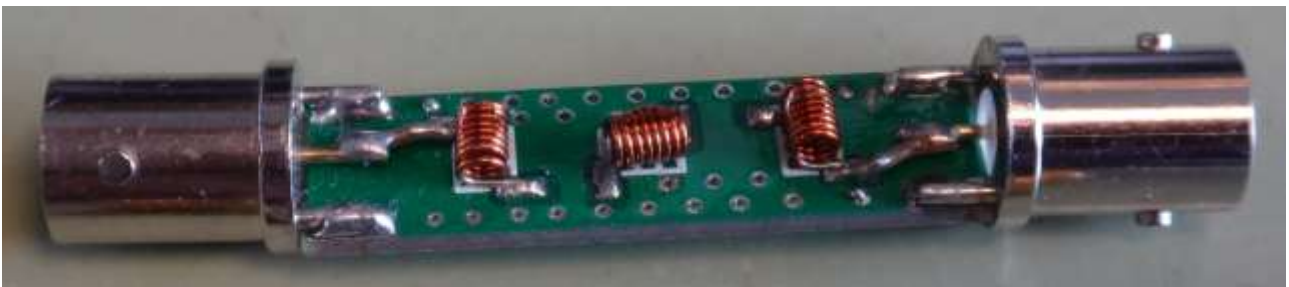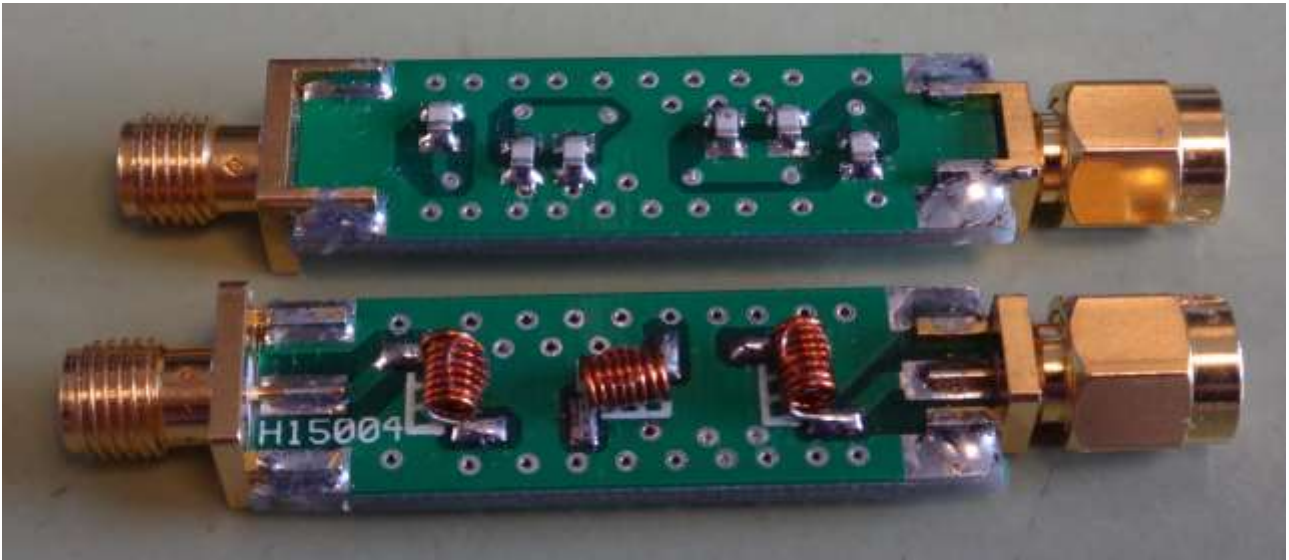

Lowpass filter with BNC connectors for PCB Tyco 5-1634503-1 (Farnell 1020980)

If C1-C6 are replaced with 33pF COG/NPO 200V Size 805 (Farnell 2332725)

attenuation at 288 MHz is increased from 56 dB to 68 dB but insertion loss at 145 MHz will increase from 0.4 dB to 0.8 dB.

OZ4HZ , Hans